
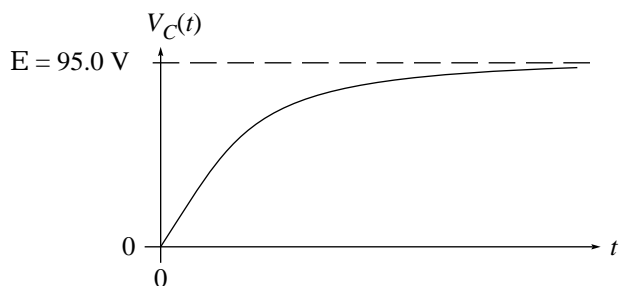


An application for RC circuits

A capacitor charging (no lamp)

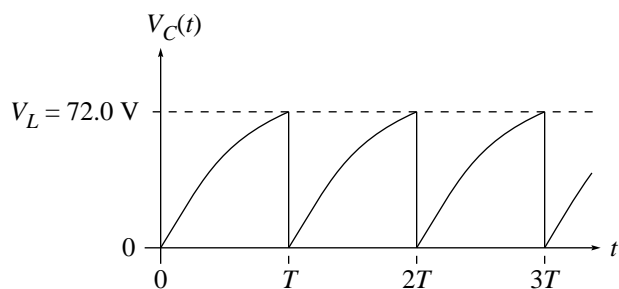

This circuit (with lamp)



During the rise (that is, for $0 < t < T$) the voltage across the capacitor is (see LSM, page 456, last equation in caption for figure 10.39)

$$V_C(t) = \mathcal{E} \left(1 - e^{-t/RC} \right).$$

I select the period T by demanding that

$$V_L = \mathcal{E} \left(1 - e^{-T/RC} \right).$$

Solve for R :

$$\begin{aligned} \frac{V_L}{\mathcal{E}} - 1 &= -e^{-T/RC} \\ -\frac{T}{RC} &= \ln \left(1 - \frac{V_L}{\mathcal{E}} \right) \\ R &= -\frac{T}{C \ln(1 - V_L/\mathcal{E})}. \end{aligned}$$

Using $V_L = 72.0 \text{ V}$, $\mathcal{E} = 95.0 \text{ V}$, $C = 0.150 \mu\text{F}$, and $T = 0.500 \text{ s}$, we find

$$R = 2.35 \text{ M}\Omega.$$

Grading: Starting off (e.g. a graph like these or a circuit diagram): 2 points

Exponential growth equation: 2 points

Solve for R : 2 points

Number: 2 points

Units: 1 point

Three significant figures: 1 point