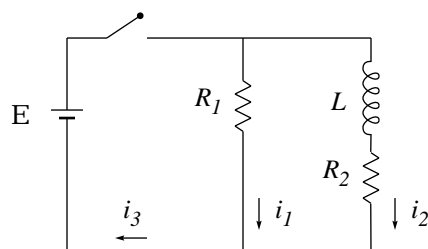


Inductor in a circuit



Condition I: Initial State. The current in branch 1 jumps instantly to its final value, while in branch 2 the inductance prevents this discontinuous shift. The inductor acts like a break in the wire.

- $i_1 = \Delta V_1 / R_1 = \mathcal{E} / R_1 = 2.0 \text{ A}$
- $i_2 = 0$
- $i_3 = i_1 + i_2 = 2.0 \text{ A}$
- $\Delta V_2 = i_2 R_2$ so, from part (b), $\Delta V_2 = 0$
- $\mathcal{E}_{\text{battery}} = \Delta V_L + \Delta V_2$, so $\Delta V_L = \mathcal{E} = 10 \text{ V}$
- $\Delta V_L = L \frac{di_2}{dt}$ so $\frac{di_2}{dt} = \frac{10 \text{ V}}{5.0 \text{ H}} = 2.0 \text{ A/s}$

Condition II: Equilibrium. A long time has passed and everything has settled down. Because the currents don't change with time, there is no voltage drop across the inductor. The inductor acts like a piece of resistanceless wire.

- $i_1 = \Delta V_1 / R_1 = \mathcal{E} / R_1 = 2.0 \text{ A}$
- $i_2 = \Delta V_2 / R_2 = \mathcal{E} / R_2 = 1.0 \text{ A}$ because $\Delta V_L = 0$
- $i_3 = i_1 + i_2 = 3.0 \text{ A}$
- $\mathcal{E}_{\text{battery}} = \Delta V_L + \Delta V_2$, so $\Delta V_2 = \mathcal{E} = 10 \text{ V}$
- $\Delta V_L = 0$
- $di_2/dt = 0$

Grading: One point for each correct letter, maximum of 10. For this problem only, no explanation is required.