Solution of the RC circuit differential equation

ODE:
$$\frac{dq(t)}{dt} + \frac{q(t)}{RC} = \frac{\mathcal{E}_m}{R}\sin(\omega t)$$
 (1)

ansatz:
$$q(t) = Q\cos(\omega t - \phi)$$
 (2)

where the Q and ϕ are adjustable parameters that will depend (in ways to be uncovered) upon R, C, ω , and \mathcal{E}_m .

Plug the ansatz into the ODE, giving

$$-Q\omega\sin(\omega t - \phi) + \frac{Q}{RC}\cos(\omega t - \phi) = \frac{\mathcal{E}_m}{R}\sin(\omega t).$$
(3)


If this equation is to hold for all times, it must hold for the time t = 0:

$$-Q\omega\sin(-\phi) + \frac{Q}{RC}\cos(-\phi) = 0$$
(4)

$$\tan\phi = -\frac{1}{\omega RC} \tag{5}$$

Define $X_C \equiv \frac{1}{\omega C}$ and call it the "reactance" or "impedance" of the capacitor (dimensions: ohm). Then

$$\tan\phi = -\frac{X_C}{R}.\tag{6}$$

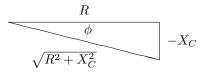

If the ansatz is to hold for all times, then it must also hold for the time when $\omega t = \phi$, at which time equation (3) becomes

$$\frac{Q}{RC} = \frac{\mathcal{E}_m}{R}\sin\phi \tag{7}$$

$$Q = \mathcal{E}_m C \sin \phi = \mathcal{E}_m C \left(-\frac{X_C}{\sqrt{R^2 + X_C^2}} \right)$$
(8)

So we've shown that if ansatz (2) is a solution to ODE (1), then the parameters Q and ϕ must take on the values given in equations (6) and (8). But we've not yet shown that ansatz (2) is *really* a solution. To do so, plug equations (6) and (8) into (3)

$$-\omega \mathcal{E}_m C \sin \phi \sin(\omega t - \phi) + \frac{\mathcal{E}_m C \sin \phi}{RC} \cos(\omega t - \phi) = \frac{\mathcal{E}_m}{R} \sin \omega t$$
(9)

$$-\omega RC\sin\phi\sin(\omega t - \phi) + \sin\phi\cos(\omega t - \phi) = \sin\omega t \tag{10}$$

and use the dreaded (at least, dreaded by me) sum angle formulas

$$\sin(\omega t - \phi) = \sin \omega t \cos \phi - \cos \omega t \sin \phi \tag{11}$$

$$\cos(\omega t - \phi) = \cos \omega t \cos \phi + \sin \omega t \sin \phi. \tag{12}$$

This gives (using $\omega RC = R/X_C$)

$$\left[-\frac{R}{X_C}\sin\phi\cos\phi + \sin^2\phi\right]\sin\omega t + \left[\frac{R}{X_C}\sin^2\phi + \sin\phi\cos\phi\right]\cos\omega t = \sin\omega t.$$
(13)

But from equation (6)

$$\sin \phi = -\frac{X_C}{\sqrt{R^2 + X_C^2}} \quad ; \quad \cos \phi = \frac{R}{\sqrt{R^2 + X_C^2}}$$
(14)

$$\sin^2 \phi = \frac{X_C^2}{R^2 + X_C^2} \quad ; \quad \sin \phi \cos \phi = -\frac{RX_C}{R^2 + X_C^2} \tag{15}$$

whence (13) becomes

$$[1]\sin\omega t + [0]\cos\omega t = \sin\omega t. \tag{16}$$

Which is manifestly true!