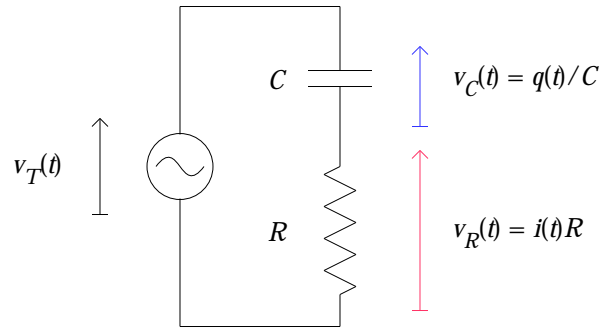


## Conclusions concerning RC circuit



In all cases:

$$v_R(t) = RC \frac{dv_C(t)}{dt}$$

Sinusoidal driving:

$$v_T(t) = \mathcal{E}_m \sin \omega t \quad \omega = 2\pi f$$

**Slow changes:**  $\left( \text{low frequencies; } f \ll \frac{1}{2RC} \right)$

- **Voltage is mostly across capacitor** ( $v_C(t) \approx v_T(t)$ ;  $v_R(t) \ll v_T(t)$ )
- $v_C(t)$  ( $\propto$  charge) lags  $v_T(t)$  by a bit
- $v_R(t)$  ( $\propto$  current) leads  $v_T(t)$  by about  $\frac{1}{4}$  period
- **Differentiation circuit:**  $v_R(t) \approx RC \frac{dv_T(t)}{dt}$   
[holds for any slowly varying  $v_T(t)$ ]

**Fast changes:**  $\left( \text{high frequencies; } f \gg \frac{1}{2RC} \right)$

- **Voltage is mostly across resistor** ( $v_R(t) \approx v_T(t)$ ;  $v_C(t) \ll v_T(t)$ )
- $v_C(t)$  ( $\propto$  charge) lags  $v_T(t)$  by about  $\frac{1}{4}$  period
- $v_R(t)$  ( $\propto$  current) leads  $v_T(t)$  by a bit
- **Integration circuit:**  $v_T(t) \approx RC \frac{dv_C(t)}{dt} \implies v_C(t) \approx \frac{1}{RC} \int v_T(t) dt$   
[holds for any rapidly varying  $v_T(t)$ ]

At all frequencies,  $v_R(t)$  leads  $v_C(t)$  by exactly  $\frac{1}{4}$  period